

Logic Design


Combinational Circuits

Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck

Problem
Algorithm
Program
Instruction Set Architecture
Microarchitecture
Logic
Digital Circuits
Analog Circuits
Devices
Physics

From the Last lecture ...


Abstractions

 

Architecture



Modern System on Chip


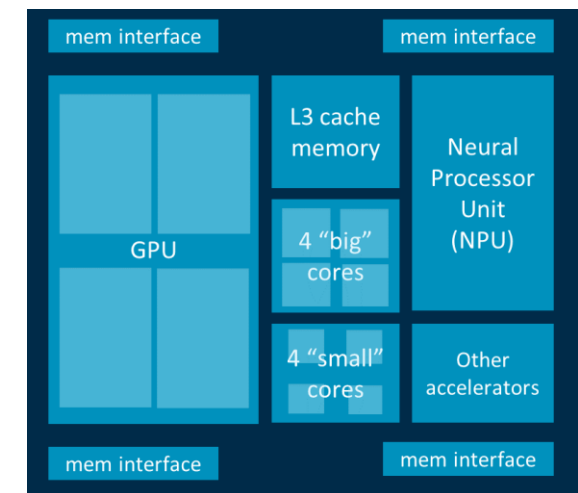


Outline

- Introduction
- Boolean Equations
- Truth Tables
- Boolean Algebra
- Gates
- Combinational Logic
 - Decoders
 - Multiplexors
 - Two-level Logic
- Hardware Description Languages
 - Verilog
 - VHDL


Introduction

 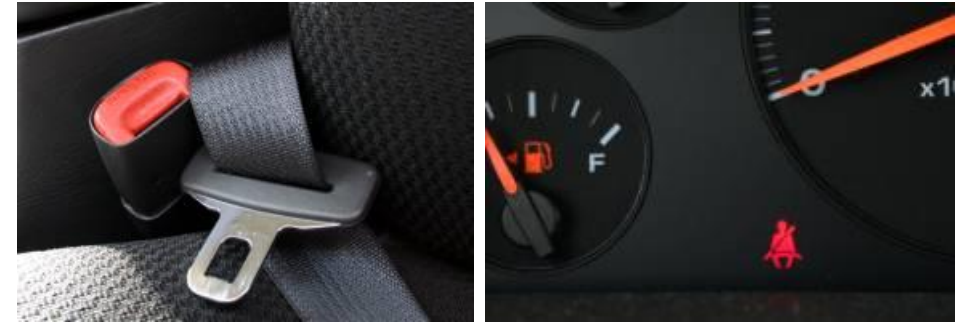- Seat Belt Warning Light System
 - Design circuit for warning light
 - Sensors
 - $s=1$: seat belt fastened
 - $k=1$: key inserted
 - $p=1$: person in seat
 - Capture Boolean equation
 - person in seat, and seat belt not fastened, and key inserted
- $$w = p \text{ AND NOT}(s) \text{ AND } k$$
- Convert equation to circuit




Logic Circuit

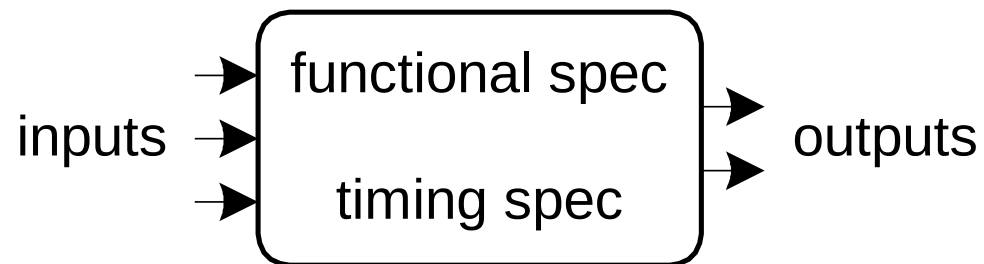- A logic circuit is composed of:
 - Inputs
 - Outputs
 - Functional specification
 - Timing specification



 
- Nodes
 - Inputs: A, B, C
 - Outputs: Y, Z
 - Internal: n1
- Circuit elements
 - E1, E2, E3 (Each a circuit)



Types of Logic Circuits

- Combinational Logic

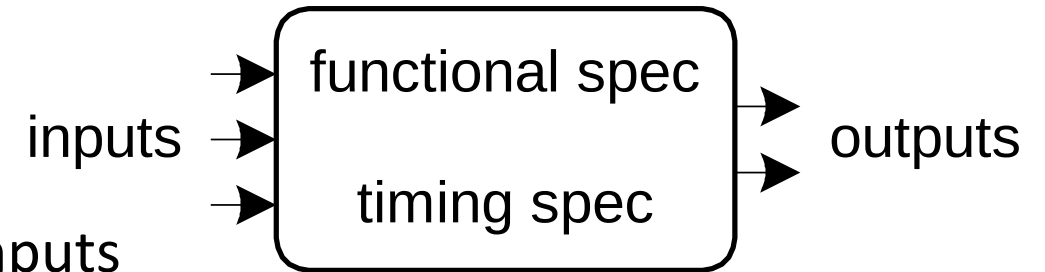- Memoryless
- Outputs determined by current values of inputs



- Sequential Logic



- Has memory
- Outputs determined by previous and current values of inputs

Boolean Algebra and its Relation to Digital Circuits

- Boolean Algebra


- Variables represent 0 or 1 only
- Operators return 0 or 1 only
- Basic operators
 - AND: A AND B returns 1 only when both A=1 and B=1
 - OR: A OR B returns 1 if either (or both) A=1 or B=1
 - NOT: NOT a returns the opposite of a (1 if A=0, 0 if A=1)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

  

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

A	F
0	1
1	0

 


Boolean Equations

- Functional specification of outputs in terms of inputs
- Example:

$$Y = F(A, B, C)$$

$$Z = F(A, B, C)$$

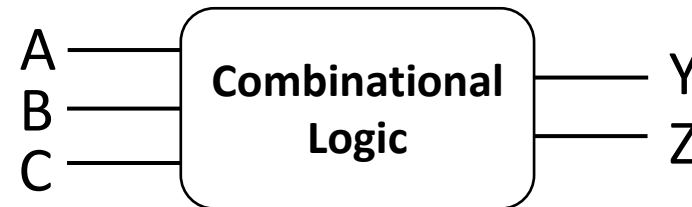

Boolean Algebra Terminology

- Example equation: **$F(A,B,C) = A'BC + ABC' + AB + C$**
- Variable
 - Represents a value (0 or 1)
 - Three variables: A, B, and C
- Literal
 - Appearance of a variable, in true or complemented form
 - Nine literals: A', B, C, A, B, C', A, B, and C
- Product term
 - Product of literals
 - Four product terms: A'BC, ABC', AB, C
- Sum-of-products
 - Equation written as OR of product terms only
 - Above equation is in sum-of-products form

Boolean Algebra Properties

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- To prove, just evaluate all possibilities

Boolean Algebra Properties – Example

- Show **$abc + abc' = ab$** .
- Use first distributive property
 - $abc + abc' = ab(c+c')$.
- Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
- Identity property
 - $ab(1) = ab*1 = ab$.
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$

Boolean Algebra: Additional Properties


- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a'b'$
 - $(ab)' = a' + b'$
 - Very useful!
- To prove, just evaluate all possibilities

Representations of Boolean Functions

- A function can be represented in different ways
 - Natural language, Equation, Circuit, and Truth Table ...
- Natural language: F outputs 1 when A is 0 and B is 0, or when A is 0 and B is 1.

- $F(A,B) = A'B' + A'B$


Is their output same?

 

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

- Natural language: F outputs 1 when A is 0, regardless of B's value

- $F(A,B) = A'$

 

Truth Table Representation of Boolean Functions

- Define value of F for each possible combination of input values

- 2-input function: 4 rows
 - 2^n

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

- 3-input function: 8 rows

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Truth Table Representation of Boolean Functions

- Use truth table to define function $F(A,B,C)$ that is 1 when ABC is 5 or greater in binary

A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Truth Table Representation of Boolean Functions

- Use truth table to define function $F(A,B,C)$ that is 1 when ABC is 5 or greater in binary

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Standard Representation: Truth Table

- How can we determine if two functions are the same?
 - Use algebraic methods
 - But if we failed, does that prove not equal? No.
- Solution: Convert to truth tables
 - Only ONE truth table representation of a given function
- Determine if **$F1=AB+A'$** is same function as **$F2=A'B'+A'B+AB$** , by converting each to truth table first

A	B	F1
0	0	1
0	1	1
1	0	0
1	1	1

$$F1=AB+A'$$

Same!


A	B	F2
0	0	1
0	1	1
1	0	0
1	1	1

$$F2=A'B'+A'B+AB$$


Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Example: $F = AB + C'$, $G = AB + BC$

 **Two-level logic:
ANDs followed by ORs**





Separate circuits

 

Shared gates

Example – BCD to 7-segment converter

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

  

$$A = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

$$B = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz + wx'y'z' + wx'y'z$$

Combinational Logic Design Process

- Capture the function
 - Create a truth table or equations, whichever is most natural for the given problem, to describe the desired behavior of the combinational logic.
- Convert to equations
 - This step is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.
- Implement as a gate-based circuit
 - For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)


Example – Number of 1s count

- Problem: Output in binary on two outputs YZ (2 bits) the number of 1s on three inputs
 - 010 -> 01 (1)
 - 101 -> 10 (2)
 - 000 -> 00 (0)
- **Step 1:** Capture the function
 - Truth table or equation?
 - Truth table is straightforward
- **Step 2:** Convert to equation
 - $Y = A'BC + AB'C + ABC' + ABC$
 - $Z = A'B'C + A'BC' + AB'C' + ABC$

A	B	C	#1s	Y	Z
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	2	1	0
1	0	0	1	0	1
1	0	1	2	1	0
1	1	0	2	1	0
1	1	1	3	1	1

 Example cont...

- **Step 3:** Implement as a gate-based circuit



Two-level logic:
ANDs followed by ORs


A	B	C	#1s	Y	Z
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	2	1	0
1	0	0	1	0	1
1	0	1	2	1	0
1	1	0	2	1	0
1	1	1	3	1	1

More Gates

- NAND: Opposite of AND (“NOT AND”)

- Use-case – Alarm circuits

 
Any boolean function can be implemented by using a combination of NAND (or NOR) gates. This property is called functional completeness.



A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

- NOR: Opposite of OR (“NOT OR”)


- Use-case – Detect all zeros!

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


More Gates cont...

 - XOR: Exactly 1 input is 1, for 2-input XOR
 - Detecting odd # of 1s
 - Useful for generating “parity” bit common for detecting errors



A	B	F
0	0	0
0	1	1
1	0	1
1	1	0


 
- XNOR: Opposite of XOR (“NOT XOR”)
 - Detecting equality



A	B	F
0	0	1
0	1	0
1	0	0
1	1	1


Multilevel Logic

  - Complex logic is often built from many stages of simpler gates




Decoders

 - Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
 - N inputs, 2^N outputs
- Internal design
 - AND gate for each output to detect input combination
- One-hot outputs: only one output **HIGH** at once



A	B	F0	F1	F2	F3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

Multiplexer (MUX)

- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux $\rightarrow$ needs 2 select inputs to indicate which input to route through
 - 8 input mux $\rightarrow$ 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects
 - Like a railyard switch




Multiplexer (MUX) cont ...


- Select input is $\log_2 N$ bits – control input

- Example


- 2:1 MUX

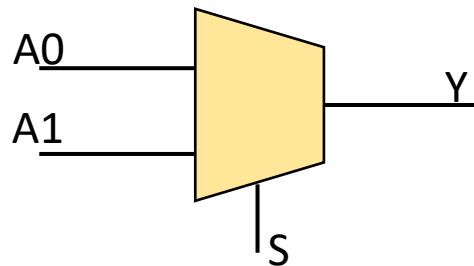

S	Y
0	A0
1	A1

 


- 4:1 MUX

 

S0	S1	Y
0	0	A0
0	1	A1
1	0	A2
1	1	A3

N-bit MUX Example

 


- Four possible display items
 - Temperature (T), Average KMs-per-litre (A), Humidity (H), and Mileage (M) -- each is 8-bits wide
 - Choose which to display using two inputs x and y
 - Use 8-bit 4x1 mux

Hardware Description Languages

- Describe hardware at varying levels of abstraction
- Structural description
 - Textual replacement for schematic
 - Hierarchical composition of modules from primitives
- Behavioral/functional description
 - Describe what module does, not how
 - Synthesis generates circuit for module
- Simulation semantics

Hardware Description Languages cont...

 - Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
 - Sim • **Modellierung digitaler Systeme auf Register-Transfer-**
 - Dela **Ebene (RTL) mit Verilog HDL (G) 03-IMGS-RTL**
 - Fair • **SoSe 23**
 - IEEE standard



```
module m41 ( I0, I1, I2, I3, s0, s1, D);
```

```
input wire [7:0] I0;
input wire [7:0] I1;
input wire [7:0] I2;
input wire [7:0] I3;
```

```
input wire [7:0] s0;
input wire [7:0] s1;
```

```
output reg [7:0] D;
```

```
always @ (I0 or I1 or I2 or I3 or s0, s1)
begin
```


```
    case (s0 | s1)
        2'b00 : D <= I0;
        2'b01 : D <= I1;
        2'b10 : D <= I2;
        2'b11 : D <= I3;
    endcase
```

```
end
```

```
endmodule
```

Hardware Description Languages cont...

 - VHDL (circa 1987) - DoD sponsored standard
 - Similar to Ada (emphasis on re-use and maintainability)
 - Simulation semantics visible
 - Very general but verbose
 - IEEE standard



```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux_4to1 is
port(
    I0,I1,I2,I3 : in std_logic_vector (7 downto 0);
    S0,S1: in STD_LOGIC;
    D: out std_logic_vector (7 downto 0)
);
end mux_4to1;
  
```

```

architecture bhv of mux_4to1 is
begin
process (I0,I1,I2,I3,S0,S1) is
begin
    if (S0 ='0' and S1 = '0') then
        D <= I0;
    elsif (S0 ='1' and S1 = '0') then
        D <= I1;
    elsif (S0 ='0' and S1 = '1') then
        D <= I2;
    else
        D <= I3;
    end if;
end process;
end bhv;
  
```

Logic Design

Combinational Circuits

Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck

Problem
Algorithm
Program
Instruction Set Architecture
Microarchitecture
Logic
Digital Circuits
Analog Circuits
Devices
Physics

Literature

- D. Patterson, J. Hennessy: Computer Organization and Design RISC-V Edition – The Hardware Software Interface, Elsevier, 2020.
- S. L. Harris, D. Harris: Digital Design and Computer Architecture, RISC-V Edition, Elsevier, 2021.
- ARM University program: Introduction-to-Computer-Architecture-Education.
- J. Teich, C. Haubelt: Digitale Hardware/Software-Systeme – Synthese und Optimierung, Springer Verlag, 2. Auflage, 2007.
- G. De Micheli: Synthesis and Optimization of Digital Circuits, McGraw-Hill, 1994.
- G. D. Hachtel, F. Somenzi: Logic Synthesis and Verification Algorithms, Kluwer, 1996.

Literature

- H. Bähring, J. Dunkel, G. Rademacher: Mikrorechner-Systeme: Mikroprozessoren, Speicher, Peripherie, Springer-Verlag, 2. Auflage, 1994.
- J. P. Hayes: Computer Architecture and Organization, McGraw-Hill, 1998.
- M. G. Arnold: Verilog Digital Computer Design: Algorithms to Hardware, Prentice Hall, 1998.
- A. Tanenbaum: Structured Computer Organization, Prentice Hall, 5th Edition, 2006.
- D. A. Patterson, J. L. Hennessy: Computer Organization and Design - The Hardware/Software-Interface, Morgan Kaufmann, 3. Auflage, 2007.
- J. L. Hennessy, D. A. Patterson: Computer Architecture - A Quantitative Approach, Morgan Kaufmann, 4. Auflage, 2007.
- H. Kaeslin: Digital Integrated Circuit Design, From VLSI to CMOS Fabrication, Cambridge University Press, 2008.
- A. Biere, D. Kroening, G. Weissenbacher, C. M. Wintersteiger: Digitaltechnik – Eine praxisnahe Einführung, Springer-Verlag, 2008.