

Logic Design

Sequential Circuits

Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck

Problem
Algorithm
Program
Instruction Set Architecture
Microarchitecture
Logic
Digital Circuits
Analog Circuits
Devices
Physics

Announcements


- It's not compulsory to do exercises
 - However, highly recommended
 - Makes you eligible for Fachgespräch
- You can take oral exam without doing the exercises
- Groups registration
 - Anyone still looking for group members?

Revision

Representations of Boolean Functions



Natural language: F outputs 1 when A is 0 and B is 0, or when A is 0 and B is 1.

$$F(A,B) = A'B' + A'B$$

 


A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

Decoder

  

Multiplexers

 

Today's Outline

- Clocks
- Memory Elements
 - Latches
 - Flip-Flops
 - Registers
- Finite State Machines (FSMs)

Evolution of Technology





Some Questions ...

- Using only combinational circuits, can we develop complex systems?
 - What additional things we might require?
- Why is memory required by complex systems for performing any task?
 - E.g., robots need to remember past events, actions, and sensor readings to make informed decision (avoiding going in circles).
- Why is synchronization important in a complex system?
 - E.g., multiple sensor and actuators working simultaneously require to work in sync
 - How can we achieve it?


Introduction

  - How does traffic signal controller know whether to switch on RED or YELLOW or GREEN light?



The Notion of Clock

 
- When should the light change from one state to another?
- We need a **clock** to dictate when to change state
- Clock signal alternates between 0 & 1



- At the start of a clock cycle, system state changes
 - During a clock cycle, the state stays constant
 - In traffic light example, we are assuming the traffic light stays in each state an equal amount of time


The Notion of Clock cont...

 - **Clock** is a general mechanism that **triggers transition from one state to another** in a sequential circuit
- Clock **synchronizes state changes** across many sequential circuit elements
- Combinational logic evaluates for the length of the clock cycle
- Clock cycle should be chosen to accommodate maximum combinational circuit delay



Role of Clock in Complex Systems

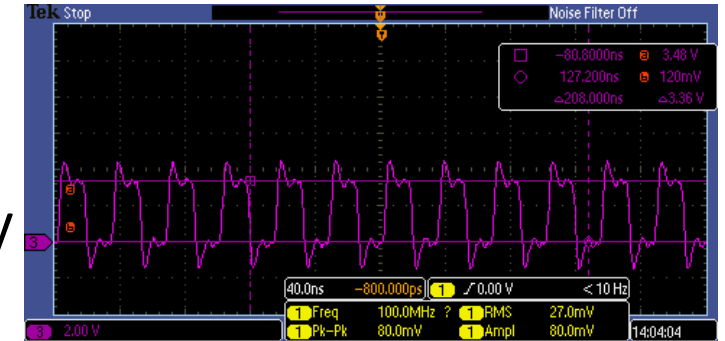- Synchronization
 - Without synchronization, data might be read incorrectly
- Timing reference
 - Allows the system to know when an event should take place
- Data transfer
 - Timing of data transfer, e.g., serial communication baud rate
- Determining speed
 - How fast a system can process data



Sequential Logic

- Outputs of sequential logic depend on current and prior input values
 - it has memory.
- Some definitions:
 - **State:** all the information about a circuit necessary to explain its future behavior
 - **Latches and flip-flops:** state elements that store one bit of state
 - **Synchronous sequential circuits:** Sequential circuits using flip-flops sharing a common clock



Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information

State Elements


- **State:** everything about the prior inputs to the circuit necessary to predict its future behavior
 - Usually just 1 bit, the last value captured
- State elements store state
 - SR Latch
 - D Latch
 - D Flip-flop
 - Registers

SR Latch
Symbol

  

SR (Set/Reset) Latch


- **SR Latch**

 

- Consider the four possible cases:
 - **$S = 1, R = 0$**
 - **$S = 0, R = 1$**
 - **$S = 0, R = 0$**
 - **$S = 1, R = 1$**

SR Latch Analysis

 
- **$S = 1, R = 0$:**
 - then **$Q = 1$** and $Q' = 0$
 - **Set the output**



A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



NOR gate

 - **$S = 0, R = 1$:**
 - then **$Q = 0$** and $Q' = 1$
 - **Reset the output**




SR Latch Analysis cont...

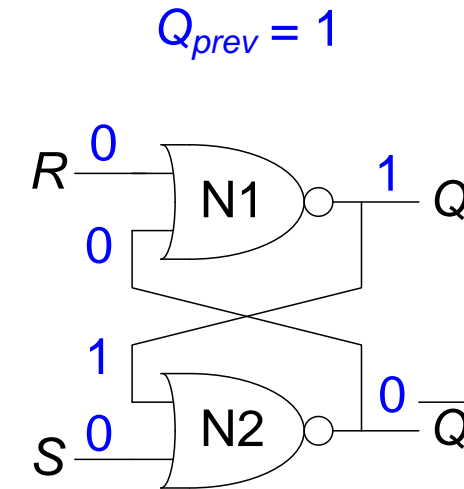 - $S = 0, R = 0$:
 - then $Q = Q_{prev}$
 - **Memory!**



A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 
- $S = 1, R = 1$:
 - then $Q = 0, \overline{Q} = 0$
 - **Invalid State**
 - $Q \neq \text{NOT } \overline{Q}$



SR Latch

- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S, R inputs
 - **Set:** Make the output 1
 - $S = 1, R = 0, Q = 1$
 - **Reset:** Make the output 0
 - $S = 0, R = 1, Q = 0$
 - **Memory:** Retain value
 - $S = 0, R = 0, Q = Q_{\text{prev}}$

SR Latch
Symbol

 


- **Must do something to avoid invalid state (when $S = R = 1$)**


D Latch

- Two inputs: CLK, D
 - CLK: controls when the output changes
 - D (the data input): controls what the output changes to
- Function
 - When CLK = 1,
 - D passes through to Q (transparent)
 - When CLK = 0,
 - Q holds its previous value (opaque)
- Avoids invalid case when
 - $Q \neq \text{NOT } \overline{Q}$

D Latch
Symbol

 

D Latch Internal Circuit


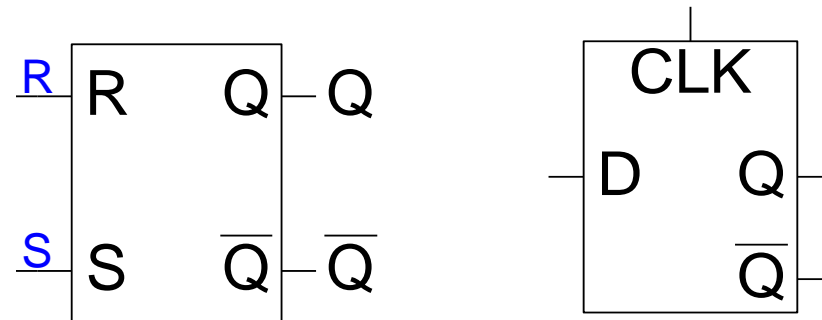


CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	$\overline{Q}_{\text{prev}}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

D Flip-Flop


- Inputs: CLK, D
- Function:
 - Samples D on **rising edge** of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK
- Called **edge-triggered**
 - Activated on the clock edge

D Flip-Flop
Symbols

  


D Flip-Flop Internal Circuit

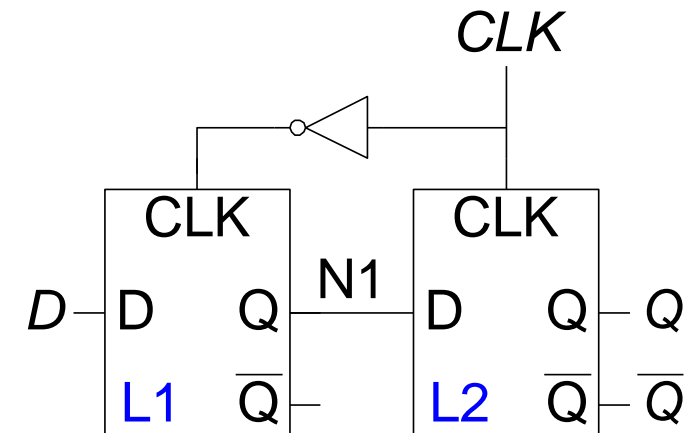
- Two back-to-back D latches (L1 and L2) controlled by complementary clocks
- When CLK = 0
 - L1 is transparent
 - L2 is opaque
 - D passes through to N1
- When CLK = 1
 - L2 is transparent
 - L1 is opaque
 - N1 passes through to Q
- Thus, on the edge of the clock (when CLK rises from 0 \rightarrow 1)
 - D passes through to Q



D Latch vs D Flip-Flop

 

D Latch

 

D Flip-flop

Synchronized to the clock

CLK

D


Q (latch)

Q (flop)


Registers

- One or more Flip-flops

Two ways to draw a register

 


4-bit Register

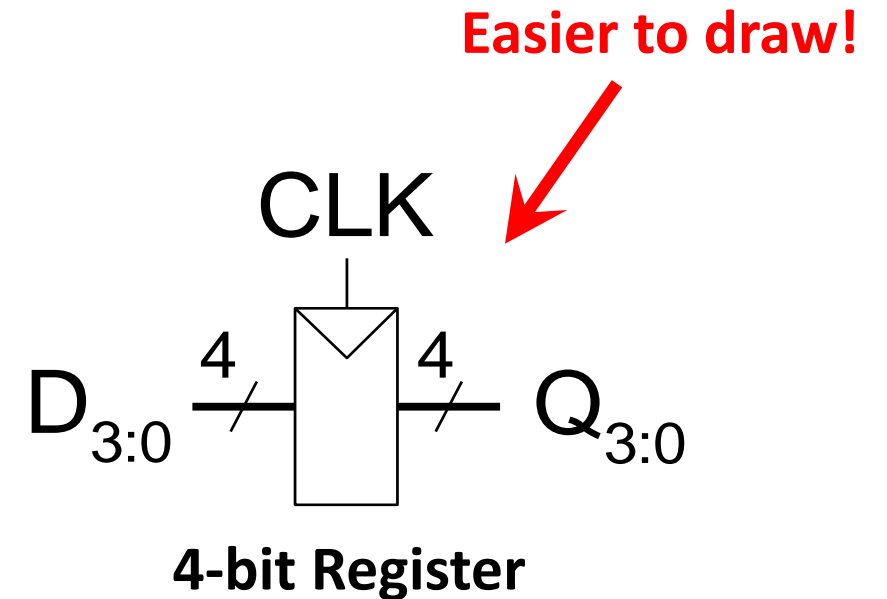

Flip-Flop with Enable

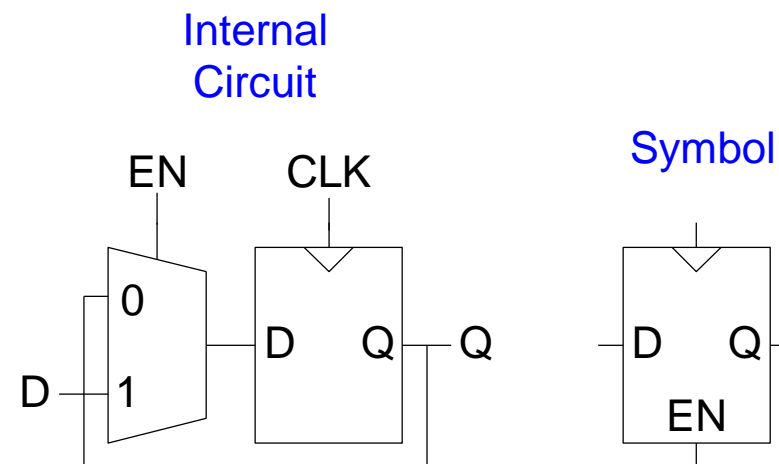
- Inputs: CLK, D, EN
 - The enable input (EN) controls when new data (D) is stored
- Function
 - EN = 1: D passes through to Q on the clock edge
 - EN = 0: the flip-flop retains its previous state



Flip-Flop with Reset


- Inputs: CLK, D, Reset
- Function:
 - Reset = 1: Q is forced to 0
 - Reset = 0: flip-flop behaves as ordinary D flip-flop

Symbols

 

Flip-Flop with Reset cont....

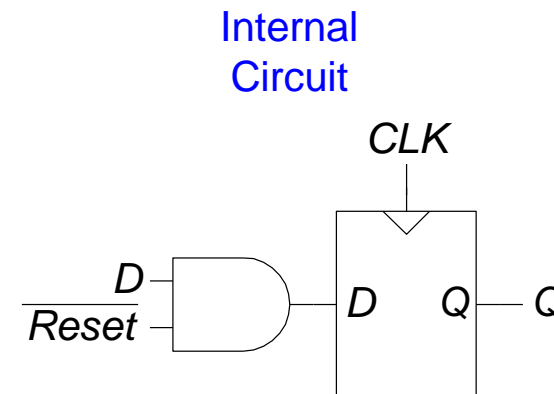- Two types:
 - Synchronous: resets at the clock edge only
 - Asynchronous: resets immediately when Reset = 1
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?



Synchronous Sequential Logic Design

- Breaks cyclic paths by inserting registers
- Registers contain state of the system
- State changes at clock edge: system synchronized to the clock
- Rules of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock
 - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
 - Finite State Machines (FSMs)
 - Pipelines (Lecture 10)

Logic Design

Sequential Circuits

Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck

Problem
Algorithm
Program
Instruction Set Architecture
Microarchitecture
Logic
Digital Circuits
Analog Circuits
Devices
Physics

Literature

- D. Patterson, J. Hennessy: Computer Organization and Design RISC-V Edition – The Hardware Software Interface, Elsevier, 2020.
- S. L. Harris, D. Harris: Digital Design and Computer Architecture, RISC-V Edition, Elsevier, 2021.
- ARM University program: Introduction-to-Computer-Architecture-Education.
- J. Teich, C. Haubelt: Digitale Hardware/Software-Systeme – Synthese und Optimierung, Springer Verlag, 2. Auflage, 2007.
- G. De Micheli: Synthesis and Optimization of Digital Circuits, McGraw-Hill, 1994.
- G. D. Hachtel, F. Somenzi: Logic Synthesis and Verification Algorithms, Kluwer, 1996.

Literature

- H. Bähring, J. Dunkel, G. Rademacher: Mikrorechner-Systeme: Mikroprozessoren, Speicher, Peripherie, Springer-Verlag, 2. Auflage, 1994.
- J. P. Hayes: Computer Architecture and Organization, McGraw-Hill, 1998.
- M. G. Arnold: Verilog Digital Computer Design: Algorithms to Hardware, Prentice Hall, 1998.
- A. Tanenbaum: Structured Computer Organization, Prentice Hall, 5th Edition, 2006.
- D. A. Patterson, J. L. Hennessy: Computer Organization and Design - The Hardware/Software-Interface, Morgan Kaufmann, 3. Auflage, 2007.
- J. L. Hennessy, D. A. Patterson: Computer Architecture - A Quantitative Approach, Morgan Kaufmann, 4. Auflage, 2007.
- H. Kaeslin: Digital Integrated Circuit Design, From VLSI to CMOS Fabrication, Cambridge University Press, 2008.
- A. Biere, D. Kroening, G. Weissenbacher, C. M. Wintersteiger: Digitaltechnik – Eine praxisnahe Einführung, Springer-Verlag, 2008.