
 


RISC-V Processor Architecture

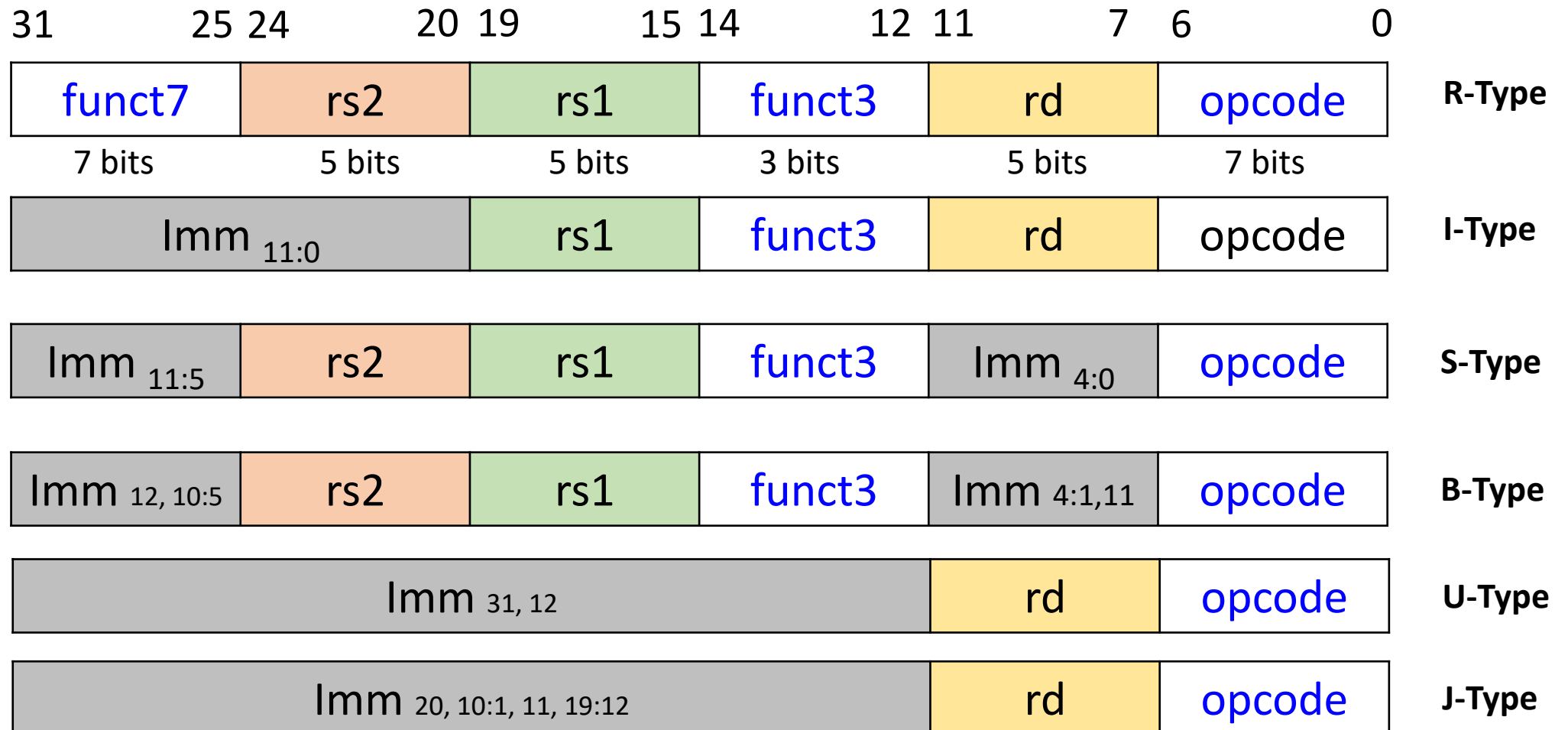Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck



Discussed the last time ...



Today's Agenda


- An Overview of RISC-V Implementation
 - Datapath
 - Controller
- Building blocks
 - Program Counter (PC)
 - Arithmetic Logic Unit (ALU)
 - Instruction Memory
 - Data Memory
 - Registers
- Implementing ADD/SUB
- Adding ADDI Instruction
 - Immediate generator

iPhone Launch




How Do We Build a Single Cycle Processor?

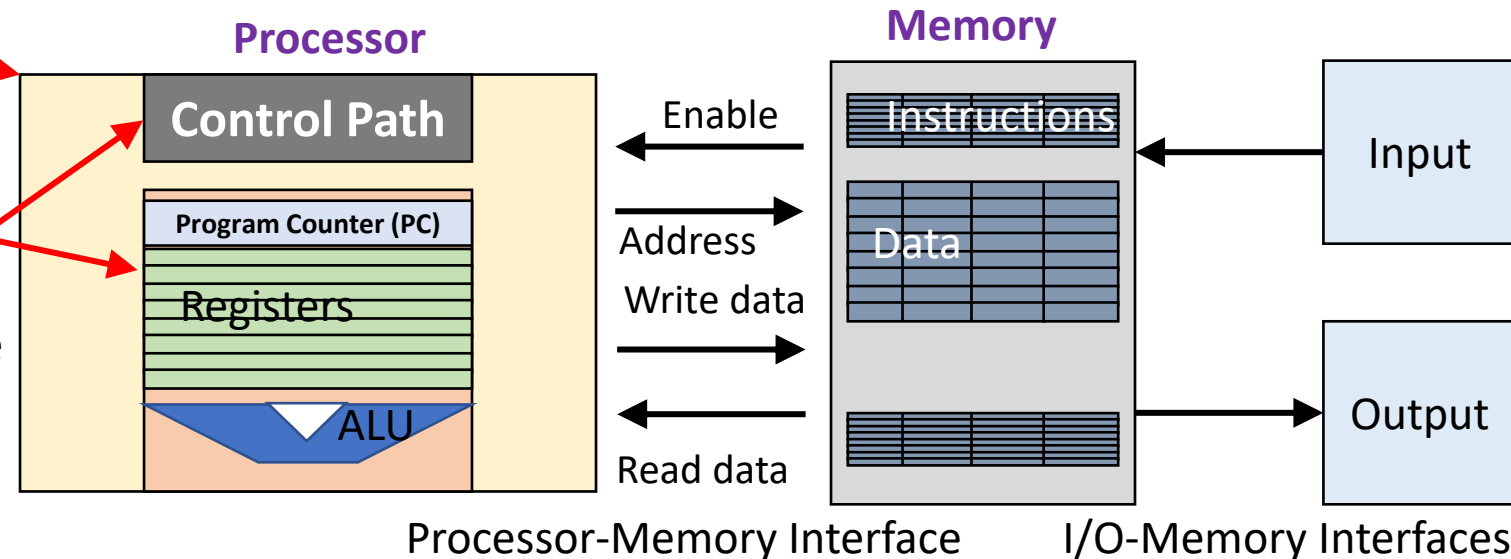- Processor (CPU)
 - The active part of the computer that does all the work (data manipulation and decision making)
- Datapath (“the brawn”)
 - portion of the processor that contains hardware necessary to perform operations required by the processor.
- Control (“the brain”)
 - portion of the processor (also in hardware) that tells the datapath what needs to be done.



Goal – Design HW to Execute All RV32I Instructions




RISC-V			RISC-V Reference Card		
Base Integer Instructions (32/64/128)			RV Privileged Instructions (32/64/128)		
Category	Name	RV32/64/128I Base	Category	Name	RV32/64/128I Base
Loads	Load Byte	LW rd, rs1, imm	CSR Access	Atomic R/W	CSRW rd, csr, rs1
	Load Halfword	LH rd, rs1, imm		Atomic Read & Set Bit	CSRCS rd, csr, rs1
	Load Word	LD rd, rs1, imm		Atomic Read & Clear Bit	CSRRC rd, csr, rs1
	Load Byte Unsigned	LBU rd, rs1, imm		Atomic R/W Imm	CSRWRI rd, csr, imm
Stores	Store Byte	SB rs1, rs2, imm	Atomic Read & Set Bit Imm	CSRRSI rd, csr, imm	
	Store Halfword	SH rs1, rs2, imm		Atomic Read & Clear Bit Imm	CSRRCI rd, csr, imm
	Store Word	SD rs1, rs2, imm			
	Store Word	SD rs1, rs2, imm			
Shifts	Shift Left	SLL rd, rs1, rs2	Change Level	Env. Call	R ERECALL
	Shift Left Immediate	SLLI rd, rs1, imm		Environment Breakpoint	R EREBP
	Shift Right	SRL rd, rs1, rs2		Environment Return	R ERETR
	Shift Right Immediate	SRLI rd, rs1, imm		Trap Redirect to Supervisor	R ERETRD
Arithmetic	ADD	ADD rd, rs1, rs2	Interrupt	Wait for Interrupt	R EREWI
	ADD Immediate	ADDI rd, rs1, imm		Supervisor Fence	R EREFENCE
	SUB	SUB rd, rs1, rs2			
	ADD Upper Imm	ADDUI rd, rs1, imm			
Logical	XOR	XOR rd, rs1, rs2	Optional Multiply-Divide Extension: RV32M		
	XOR Immediate	XORI rd, rs1, imm	Multiply	MULT	R MUL rd, rs1, rs2
	OR	OR rd, rs1, rs2		MULT Half	R MULH rd, rs1, rs2
	AND	AND rd, rs1, rs2		MULT Upper Half	R MULHU rd, rs1, rs2
Compare	Set <	SLT rd, rs1, rs2		MULT Lower Half	R MULHSU rd, rs1, rs2
	Set < Immediate	SLTI rd, rs1, imm	Divide	DIV	R DIV rd, rs1, rs2
	Set < Unsigned	SLTU rd, rs1, rs2		DIV Immediate	R DIVI rd, rs1, imm
	Set < Imm Unsigned	SLTUI rd, rs1, imm		DIV Upper Imm	R DIVUI rd, rs1, imm
Branches	Branch =	BEQ rs1, rs2, imm	Remainder	REM	R REM rd, rs1, rs2
	Branch <	BNE rs1, rs2, imm		REM Immediate	R REMI rd, rs1, imm
	Branch < Branch	BLT rs1, rs2, imm			
	Branch < Branch	BGE rs1, rs2, imm			
Jump & Link	Jump	JAL rd, imm	Optional Atomic Instruction Extension: RVA		
	Jump & Link Register	JALR rd, rs1, imm	Load	LD	R LD rd, rs1, imm
				LD Immediate	R LDI rd, rs1, imm
				LD Upper Imm	R LDUI rd, rs1, imm
System	System CALL	R ERECALL	Store	SD	R SD rs1, rs2, imm
	System BREAK	R EREBREAK		SD Immediate	R SDI rs1, rs2, imm
				SD Upper Imm	R SDUI rs1, rs2, imm
Counters	Read CYCLE	RDCYCLE rd	Swap	SWAP	R SWAP rd, rs1
	Read CYCLE Upper Half	RDCYCLEH rd		SWAP Immediate	R SWAPI rd, rs1, imm
	Read TIME	RDTIME rd		SWAP Upper Imm	R SWAPUI rd, rs1, imm
	Read TIME Upper Half	RDTIMEH rd			
CS	Read INSTR RETired	RDINSTRRET rd	Min/Max	MINIMUM	R MIN rd, rs1, rs2
	Read INSTR upper Half	RDINSTRRETU rd		MINIMUM Unsigned	R MINU rd, rs1, rs2
				MAXIMUM	R MAX rd, rs1, rs2
				MAXIMUM Unsigned	R MAXU rd, rs1, rs2

 

<https://www.sifive.com/boards/hifive-unmatched>


<https://cdn2.hubspot.net/hubfs/3020607/An%20Introduction%20to%20the%20RISC-V%20Architecture.pdf>

Combinational Logic Blocks

   


One-Instruction-Per-Cycle RISC-V Machine

- CPU is composed of two types of subcircuits
 - Combination logic blocks
 - State elements
- On every tick of the clock, the computer executes **one instruction**
 - Current outputs of the state elements drive the inputs to **combinational logic**
 - ...whose outputs settle at the inputs to the **state elements** before the next rising clock edge.
- At the **rising edge of clock**
 - All the state elements are updated with the combinational logic outputs...
 - and execution moves to the next clock cycle.

 


State Elements Required by RS32I ISA

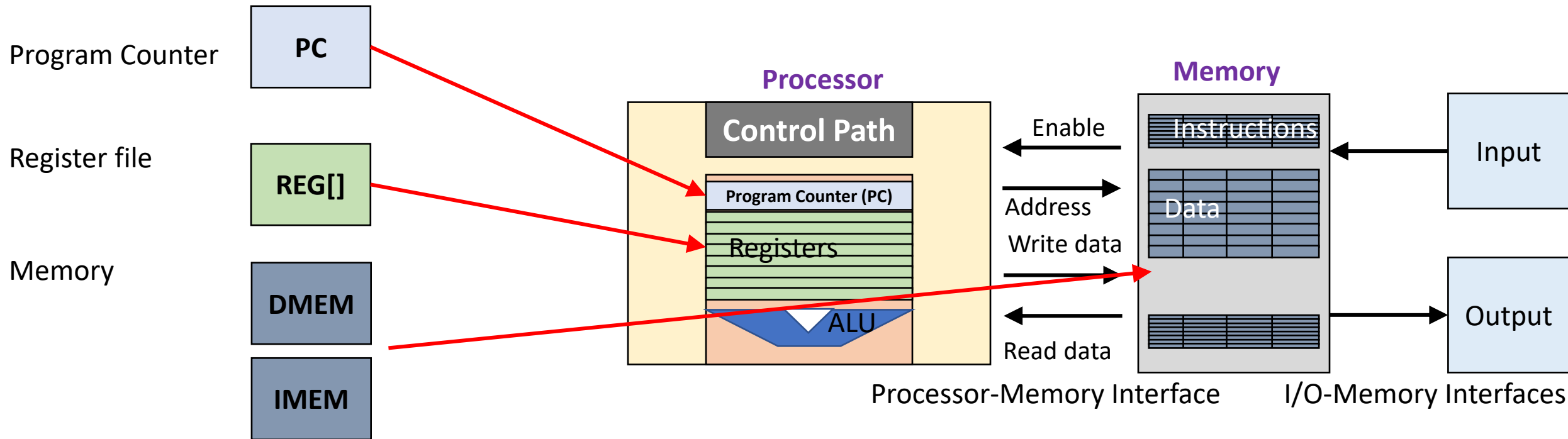

During CPU execution, each RV32I instruction reads and/or updates these state elements.

Program Counter

 - The **Program Counter** is a 32-bit register



- Input


- N-bit data input bus
- Write Enable “Control” bit (1: asserted/high, 0: deasserted/0)

- Output:

- N-bit data output bus

- Behavior:

 
- If Write Enable is 1 on **rising clock edge**, set Data Out=Data In.
- At all other times, Data Out will not change; it will output its current value.



Register File


- Input
 - One 32-bit input data bus, dataW.
 - Three 5-bit select busses, rs1, rs2, and rsW.
 - **RegWEn** control bit.
- Output
 - Two 32-bit output data busses, data1 and data2
- Registers are accessed via their 5-bit register numbers:
 - rs1 selects register to put on data1 bus out.
 - rs2 selects register to put on data2 bus out.
 - rsW selects register to be written via dataW when RegWEn=1.
- Clock behavior: Write operation occurs on rising clock edge.
 - Clock input only a factor on write!
 - All read operations behave like a combinational block:
 - If rs1, rs2 valid, then data1, data2 valid after access time.

32 Registers in RISC-V

 

Memory

- 32-bit byte-addressed memory space; and
- Memory access with 32-bit words.
- Memory words are accessed as follows:
 - Read: Address `addr` selects word to put on `dataR` bus.
 - Write: Set `MemRW=1`.
 - Address `addr` selects word to be written with `dataW` bus.
- Like `RegFile`, clock input is only a factor on write.
 - If `MemRW=1`, write occurs on rising clock edge.
 - If `MemRW=0` and `addr` valid, then `dataR` valid after access time.

 


If `MemRW=0`, MEM behaves like a combinational block.

Two Memories – IMEM and DMEM

- Current abstraction: Memory holds both instructions and data in one contiguous 32-bit memory space.


- In our processor, we'll use two "separate" memories:

 - IMEM: A read-only memory for fetching instructions.
- DMEM: A memory for loading (read) and storing (write) data words.
- Under the hood, these are placeholders for caches. (more later)




- Because IMEM is read-only, it always behaves like a combinational block:

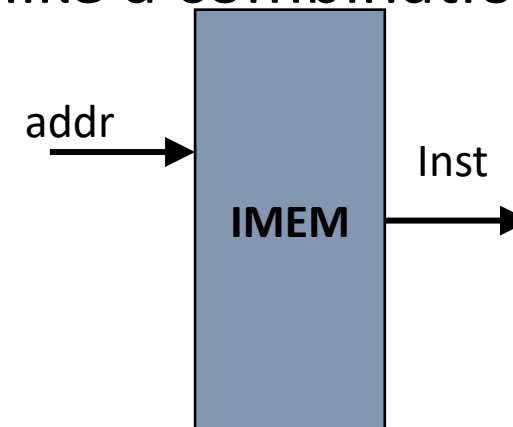- If **addr** valid, then **instr** valid after access time.




Design the Datapath in Phases

 - Task – Execute an instruction
 - All necessary operations, starting with fetching the instruction.
- Problem – A single **monolithic** block would be bulky and inefficient
- Solution – Break up the process into **stages**, then connect the stages to create the whole datapath
 - Smaller stages are easier to design!
 - **Modularity**: Easy to optimize one stage without touching the others.



Stages of Instruction Execution

- 5 basic stages

 


1. Instruction
Fetch (IF)

2. Instruction
Decode (ID)
+ Read Registers

3. Execute (EX)
Arithmetic Logic
Unit (ALU)

4. Memory
Access (MEM)

5. Write back
to Register (WB)

 


We will implement a single-cycle processor

All stages of one RV32I instruction execute within the same clock cycle.

Not All Instructions Need 5 Stages

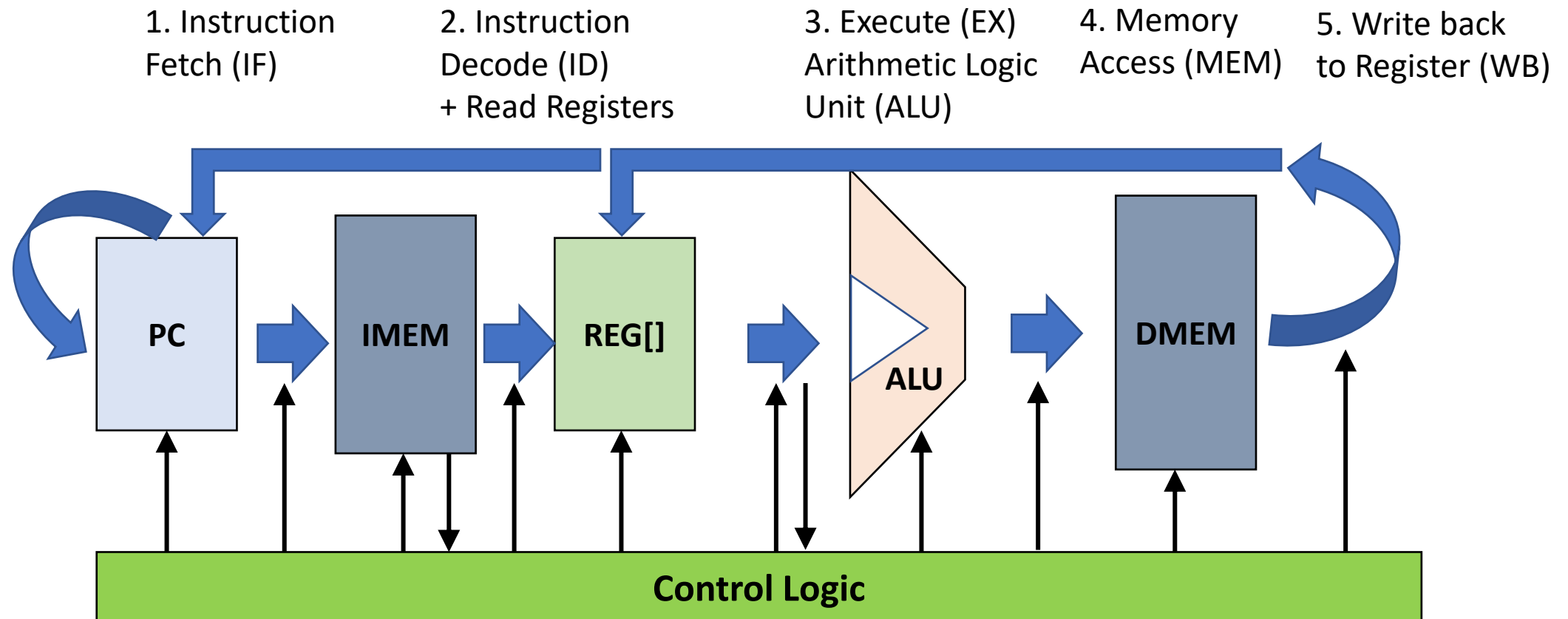- The control logic selects **needed** datapath lines based on the instruction
 - MUX selector, ALU op selector, write enable, etc.



Implementing the add Instruction

Example add-only program

0x100 | add x18,x18,x10

0x108 | add x18,x18,x18

- Suppose we had a single instruction in our RISC-V ISA

- add **add rd, rs1, rs2**

31	25 24	20 19	15 14	12 11	7 6	0
funct7	rs2	rs1	funct3	rd	opcode	
0000000	rs2	rs1	000	rd	0110011	

R-Type

The **add** instructions makes **two changes** to the processor state

- RegFile $\text{Reg}[\text{rd}] = \text{Reg}[\text{rs1}] + \text{Reg}[\text{rs2}]$
- PC $\text{PC} = \text{PC} + 4$

Datapath for add


PC = PC + 4

Increment PC to next instruction.


Split instruction to index into RegFile.

$R[rd] = R[rs1] + R[rs2]$
Feed read register values into ALU.

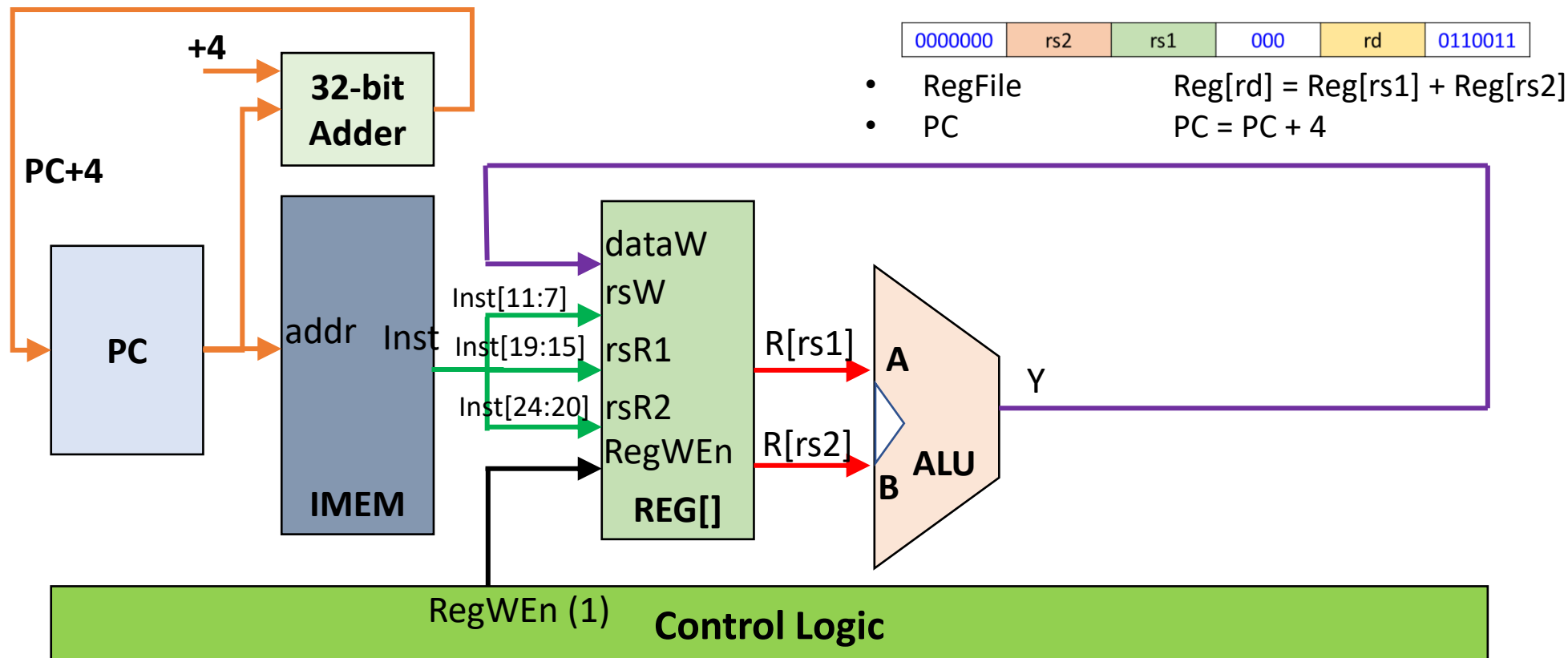Write ALU output to destination register.



Create Full Datapath Step-by-Step

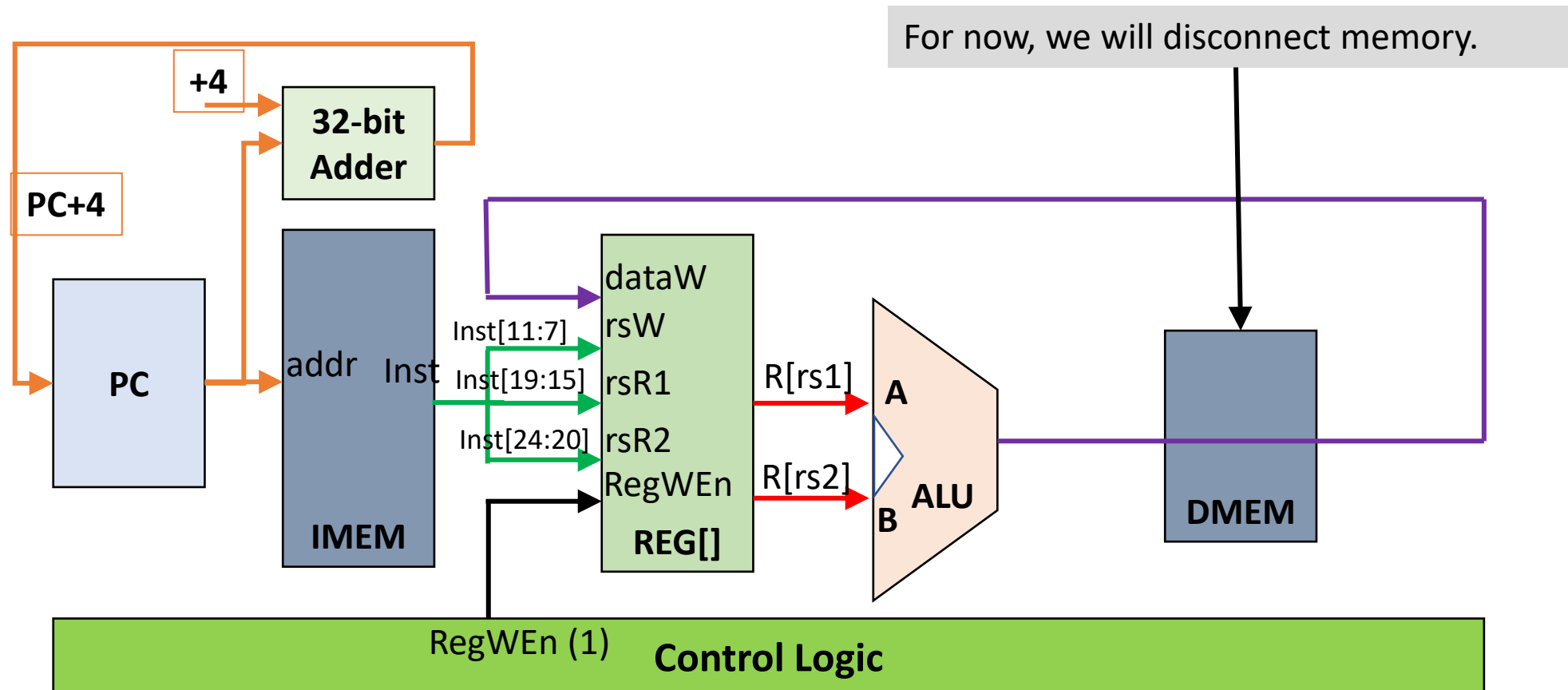

Implementing the sub Instruction

- Now we support two instructions in our RISC-V ISA
 - add/sub

31	25 24	20 19	15 14	12 11	7 6	0	
funct7	rs2	rs1	funct3	rd	opcode		
0000000	rs2	rs1	000	rd	0110011		add
0100000	rs2	rs1	000	rd	0110011		sub

sub rd, rs1, rs2

- Instruction bit **inst[30]** selects between add/sub
- Details left to control logic

sub is same as **add**, ALU subtracts operands instead of adding them

- RegFile $\text{Reg}[\text{rd}] = \text{Reg}[\text{rs1}] - \text{Reg}[\text{rs2}]$
- PC $\text{PC} = \text{PC} + 4$

Datapath for sub

0100000	rs2	rs1	000	rd	0110011
---------	-----	-----	-----	----	---------


PC = PC + 4

Increment PC to next instruction.

Split instruction to index into RegFile.

$R[rd] = R[rs1] - R[rs2]$
Feed read register values into ALU.

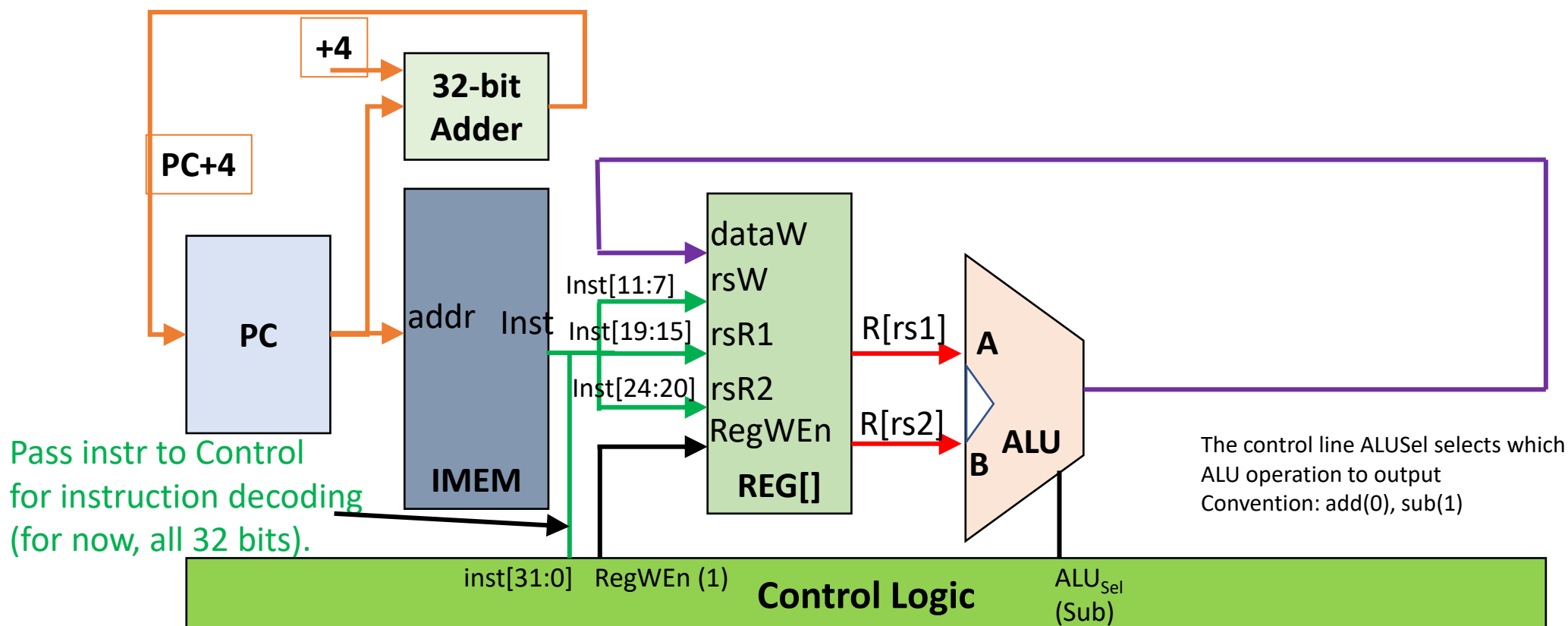Write ALU output to destination register.



Supporting All R-Type Instructions

funct7	rs2	rs1	funct3	rd	opcode	
0000000	rs2	rs1	000	rd	0110011	add
0100000	rs2	rs1	000	rd	0110011	sub
0000000	rs2	rs1	001	rd	0110011	sll
0000000	rs2	rs1	010	rd	0110011	slt
0000000	rs2	rs1	011	rd	0110011	sltu
0000000	rs2	rs1	100	rd	0110011	xor
0000000	rs2	rs1	101	rd	0110011	srl
0100000	rs2	rs1	101	rd	0110011	sra
0000000	rs2	rs1	110	rd	0110011	or
0000000	rs2	rs1	111	rd	0110011	and

The Control Logic decodes funct3, funct7 instruction fields and selects appropriate ALU function by setting the control line ALU_{Sel}

Implementing the addi Instruction

- Let's add a new instruction
 - addi

Imm _{11:0}	rs1	funct3	rd	opcode
Imm _{11:0}	rs1	000	rd	0010011


I-Type

addi rd, rs1, imm

addi updates the same two states as before. But now we need to build **immediate imm**

- RegFile $\text{Reg}[\text{rd}] = \text{Reg}[\text{rs1}] + \text{imm}$
- PC $\text{PC} = \text{PC} + 4$

Datapath for addi

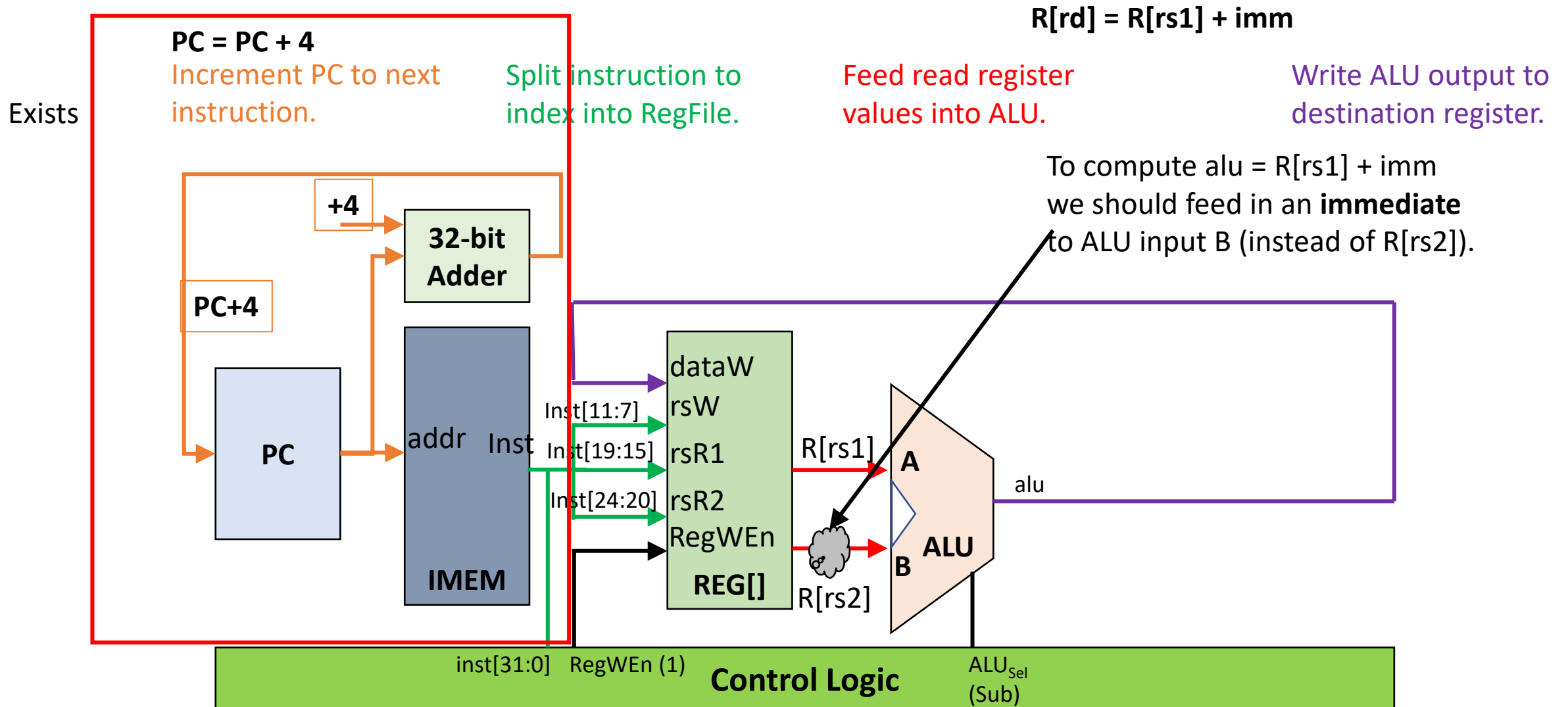

New Mux to Select Immediate for ALU

PC = PC + 4


Increment PC to next instruction.

Split instruction to index into RegFile.


Feed read register values into ALU.

Write ALU output to destination register.

$$R[rd] = R[rs1] + \text{imm}$$

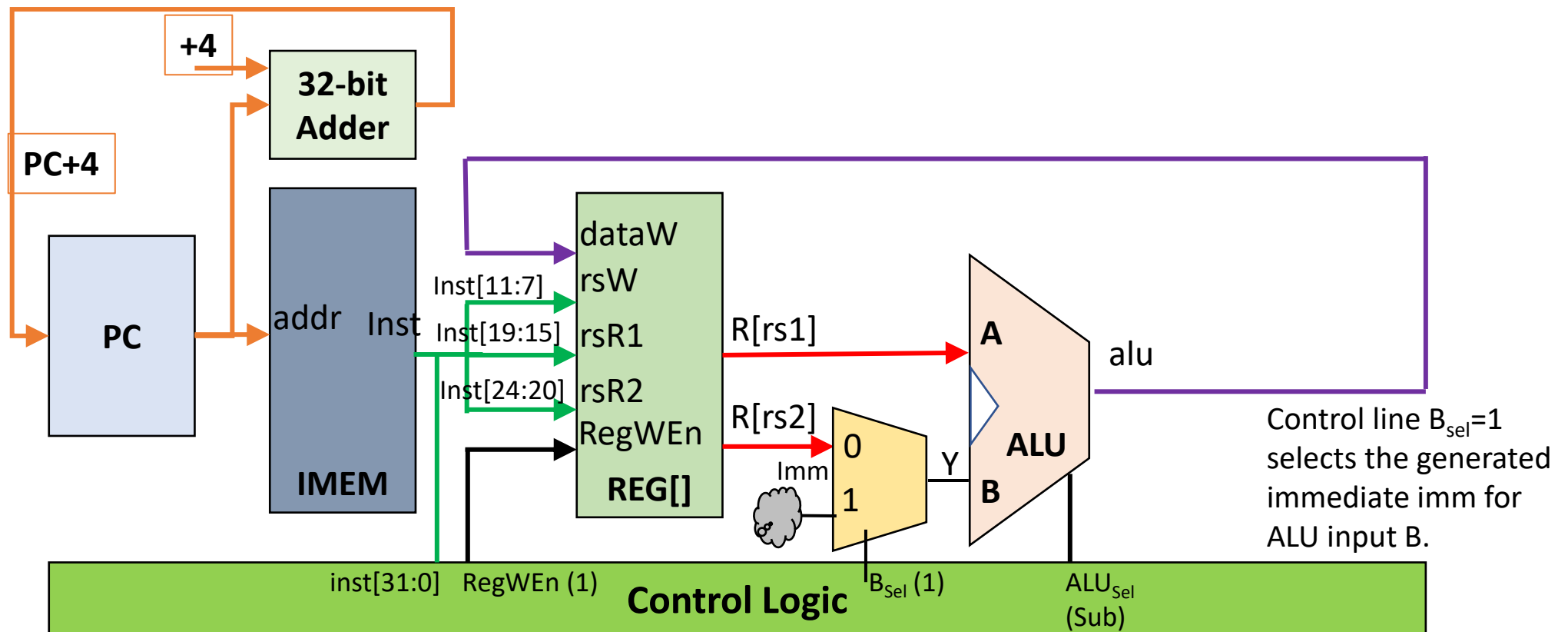


New Block to Generate 32-bit Immediate

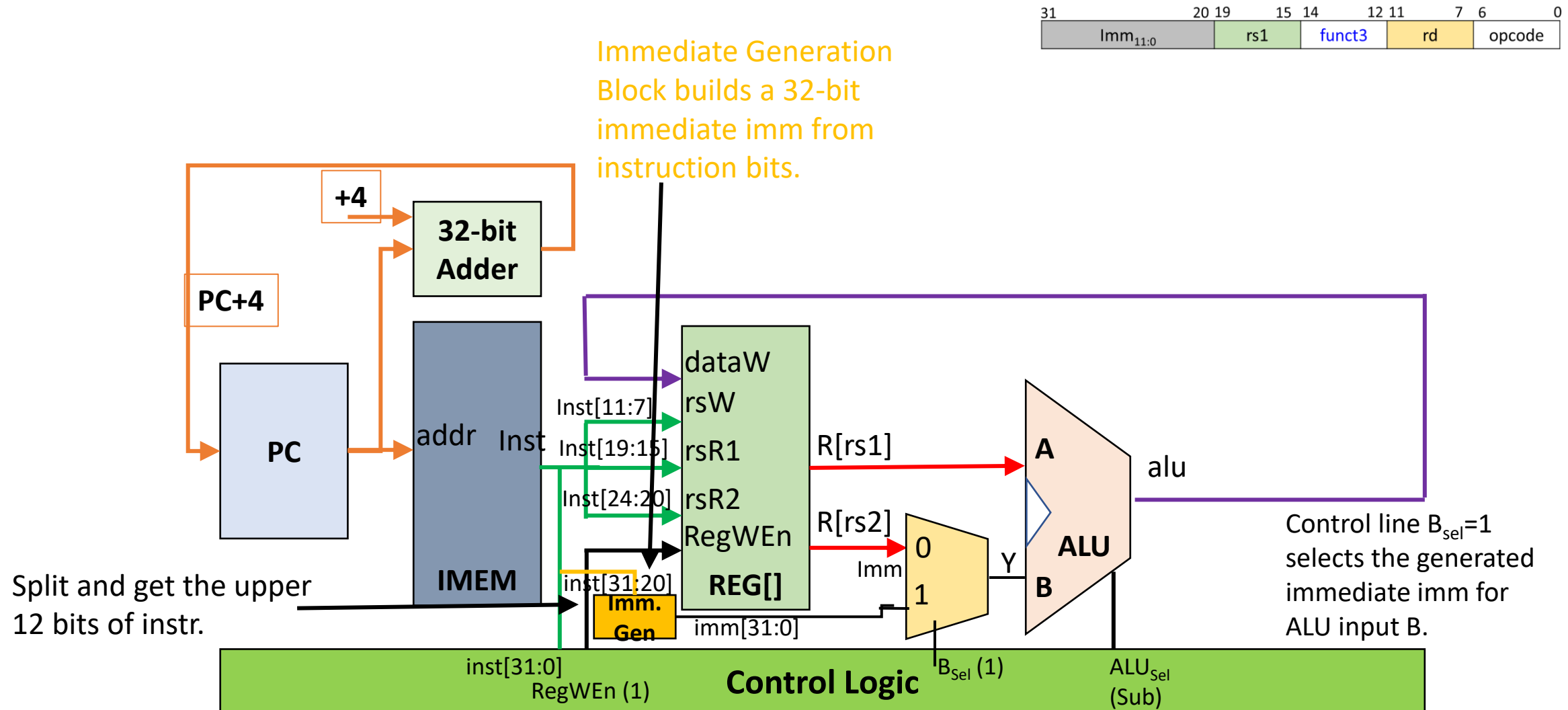

Summary

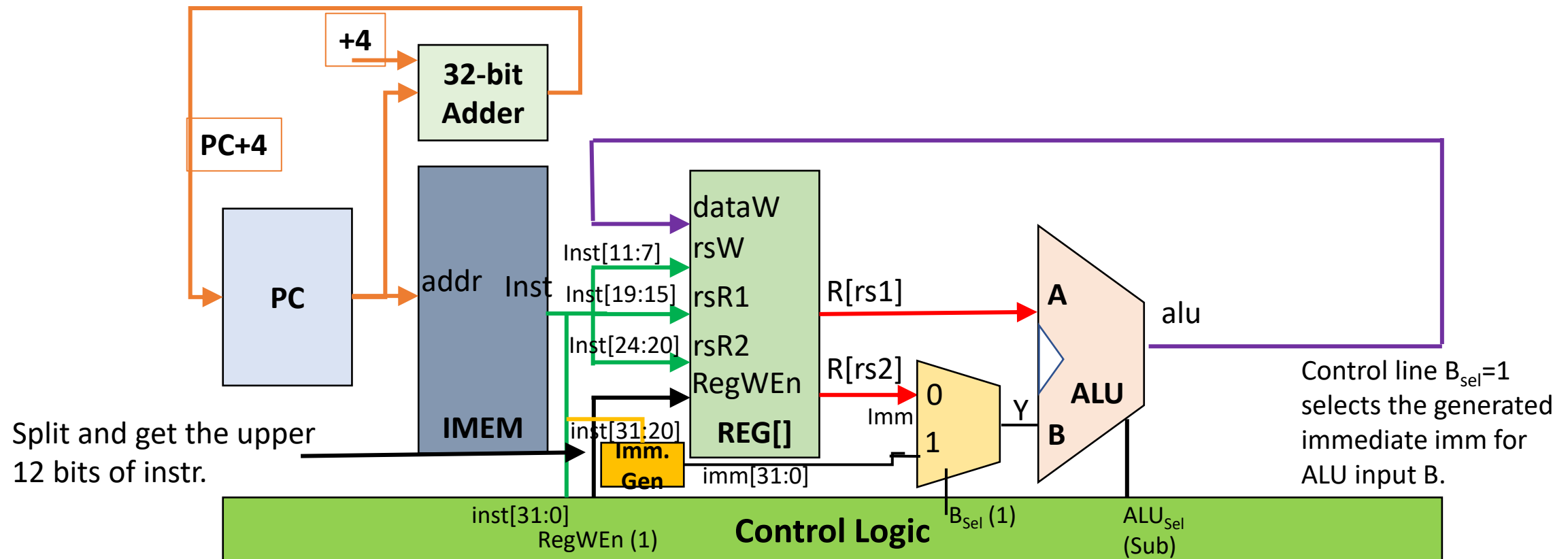- All data lines carry information
- Control logic determines what is useful/needed vs. what is ignored
 - e.g., ALUSel: chooses ALU operation; Bsel: chooses register/immediate for ALU input B.



RISC-V Processor Architecture

Prof. Dr. Rolf Drechsler
Dr. Muhammad Hassan
M.Sc. Jan Zielasko
M.Sc. Milan Funck

